

KABARAK

UNIVERSITY

**UNIVERSITY EXAMINATIONS
MAIN CAMPUS**

FIRST SEMESTER, 2019/2020 ACADEMIC YEAR

**EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN
TELECOMMUNICATION , BACHELOR OF EDUCATION SCIENCE, BACHELOR OF
SCIENCE IN COMPUTER FORENSICS, BACHELOR OF SCIENCE IN COMPUTER
SCIENCE**

PHYS 120: BASIC ELECTRONICS

STREAM: Y1S2

TIME: 9:00-11:00AM

EXAMINATION SESSION: SEP-DEC

DATE: 4/12/2019

INSTRUCTIONS TO CANDIDATES

- 1. Answer Question 1 and any other two questions in the answer booklet provided.**
- 2. Do not write on your question papers. All rough work should be done in your answer booklet.**
- 3. Clearly indicate which question you are answering.**
- 4. Write neatly and legibly.**
- 5. Edit your work for language and grammar errors.**
- 6. Follow all the instructions in the answer booklet**

*As members of Kabarak University family, we purpose at all times and in all places, to set apart in
one's heart, Jesus as Lord. (1 Peter 3:15)*



Kabarak University is ISO 9001:2015 Certified

SECTION A: (Compulsory) TOTAL MARKS FOR THIS SECTION IS 30.

Question 1 (30 marks)

- a) Explain the difference between a PNP and an NPN transistor. [2]
- b) Why are metals better conductors of electricity than semiconductors? [2]
- c) You are given figure 1 below. Copy the diagram and label it to obtain
- i. pnp transistor [2]
 - ii. npn transistor [2]

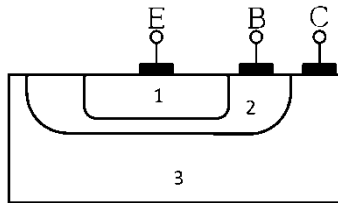


Figure 1

- d) What is the source of the leakage current in a transistor? [1]
- e) Give two examples for each of the following:
- i) donor impurity. [2]
 - ii) acceptor impurity. [2]
- f) Determine the diode current at 20°C for a silicon diode with $I_s = 0.1$ A at a reverse-bias potential of 10 V. Take: Fundamental charge $q = 1.6 \times 10^{-19}$ C; Boltzmann's constant $K_B = 1.38 \times 10^{-23}$ J/K. [4]
- g) Determine α_{DC} of a transistor if $I_E = 2.8$ mA and $I_B = 20 \mu\text{A}$. [3]
- h) Justify the following statements giving specific examples:
- i. "Semiconductor devices can serve as source of power". [2]
 - ii. "Semiconductor based devices saves energy" [2]
- i) In Figure 2, $V_{in} = 12$ Volts.
- i. Give the name of the circuit. [1]
 - ii. Explain the operation of the circuit. [3]
 - iii. Find voltage across AB. [2]

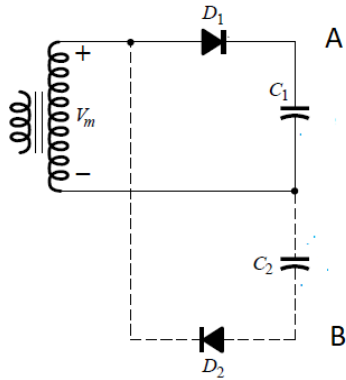


Figure 2

SECTION B. TOTAL MARKS FOR THIS SECTION IS 40.

ANSWER ANY TWO QUESTIONS FROM THIS SECTION. EACH QUESTION IN THIS SECTION CARRIES 20 MARKS.

Question 2 (20 marks)

- Draw the 2D structure illustrating bonding Ge and explain why it is an insulator at 0K. [5]
- Describe the difference between n -type and p -type semiconductor materials. [6]
- Draw a voltage regular circuit and explain its operation. [6]
- Determine I_D , and V_o for the circuit of Fig. 3. Take the threshold of silicon to be 0.6 V. [3]

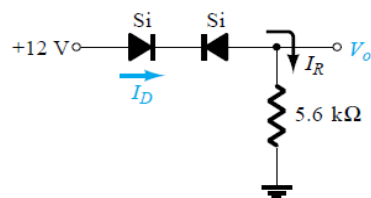


Figure 3

Question 3 (20 marks)

- Using the characteristics of Fig. 4: Find
 - The value of I_C corresponding to $V_{BE}=750$ mV and $V_{CE}= 5$ V. [2]
 - The value of V_{CE} and V_{BE} corresponding to $I_C =3$ mA and $I_B =30$ μ A. [2]
 - The dc beta at an operating point of $V_{CE}= 8$ V and $I_C =2$ mA. [3]

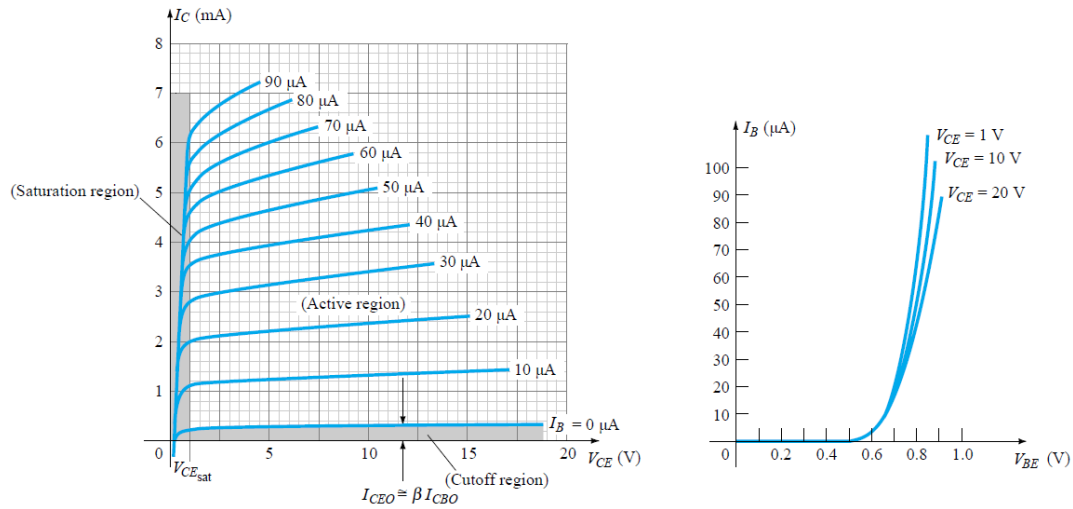


Figure 4

- b) Explain the desired bias condition for the three labeled operating points in Figure 4. [6]
- c) Determine the Q point for the circuit below (Figure 5): [7]


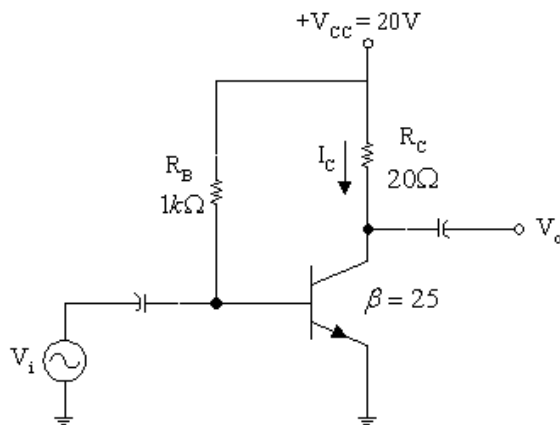


Figure 5

Question 4 (20 marks)

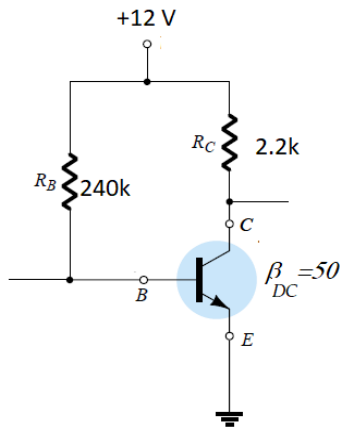- a) Define the Q point of of a transistor circuit. [2]
- b) Explain factors which affect the Q point of a transistor circuit. [4]
- c) A Fixed Bias circuit is presented in Figure 6.
- Show that the bias method is unstable. [5]
 - Draw its load line and mark the Q-point. (Take $V_{BE}=7 V$). [9]



Question 5 (20 marks)

- Draw a well-biased circuit –n channel JFET and sketch the transfer curve defined by $I_{DSS} = 12 \text{ mA}$ and $V_P = 6 \text{ V}$. [8]
- Use transistor equations to draw similarities between JFET and BJT [6]
- Derive the voltage gain of an amplifier with feedback. [6]