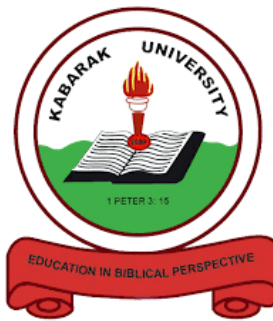


KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS

FIRST SEMESTER, 2019/2020 ACADEMIC YEAR

**EXAMINATION FOR THE DEGREE OF BACHELOR SCIENCE IN COMPUTER
SCIENCE**

COMP 213: DIGITAL CIRCUIT DESIGN

STREAM: Y2S1

TIME:9:00-11:00PM

EXAMINATION SESSION: DEC

DATE: 16/12/2019

VENUE: AUDITORIUM

COPIES: 35

INSTRUCTIONS TO CANDIDATES

- 1. Answer Question 1 and any other two questions in the answer booklet provided.**
- 2. Do not write on your question papers. All rough work should be done in your answer booklet.**
- 3. Clearly indicate which question you are answering.**
- 4. Write neatly and legibly.**
- 5. Edit your work for language and grammar errors.**
- 6. Follow all the instructions in the answer booklet**

*As members of Kabarak University family, we purpose at all times and in all places, to set apart in one's heart,
Jesus as Lord. (1 Peter 3:15)*



Kabarak University is ISO 9001:2015 Certified

QUESTION ONE (30 marks)

- a) Explain the use of buffers in digital electronics (2mks)
- b) What is the difference between decoder and a demultiplexer? (2mks)
- c) What makes it appropriate for digital systems such as computers to work on binary variables in their operations? (2mks)
- d) Explain any three disadvantages of analog signals over digital signal (3mks)
- e) Explain the NAND gate giving its logic equation and all the possible outputs in a truth table. (5mks)
- f) Explain the duality of De-Morgans Theorem (2mks)
- g) Draw the block diagram of half adder giving the equations for the outputs with their truth table (5mks)
- h) If a 3-input XNOR gate has eight input possibilities, show all the possibilities with their respective outputs (4mks)
- i) Define Programmable Logic Devices (PLDs). Draw a Programmed Array Logic to implement the following equation. $Y=A'B'+A'B+AB$ (5Mks)

QUESTION TWO (20 marks)

- a) Consider the following function $F=x'y'z+x'yz+xy'$
 - i) Minimize the function to give equivalent simpler function (3mks)
 - ii) Draw the logic gates before and after simplification. (4mks)
 - iii) How many gates do you save from this simplification (2mks)
 - b) Give any three applications of encoders (3mks)
 - c) Draw the block diagram for S-R latch using NAND gate.
- What happens when all the inputs are '1'? (4mks)
- d) Prove that $A(B+C) = (A B) + (A C)$ (4mks)

QUESTION THREE (20 marks)

- a) Explain any three differences between combinational and sequential circuits (3mks)
- b) What is the difference between an encoder and a multiplexer (2mks)
- c) Use the Boolean algebra to reduce the following equation
$$F=(x'+y'+x'y'+xy)(x'+yz)$$
 (4mks)
- d) Show that $(a + b)(a + c)$ is logically equivalent to $a + bc$. Draw the logic circuits for each (6mks)
- e) What is the importance of a clock in a flip flop (2mks)
- f) Draw the symbol and the equation for XOR gate (3mks)

QUESTION FOUR (20 marks)

- a) Explain the use of exclusive-OR in the design of full adder (3mks)
- b) To reduce the number of intergrated circuits, multiplexer is used. Explain how a 4-line to 1-line multiplexer works (4mks)
- c) Simplify the following expression using a Karnaugh map:

$$A.\bar{B}.\bar{C} + \bar{A}.B.\bar{C} + A.\bar{B}.C + \bar{A}.B.C$$
 (4mks)


- d) Show the map by their equivalent decimal values in the respective cells in a 4 input variable K-map (3mks)
- e) State any four postulates of Boolean algebra. (4mks)
- f) What is the equivalence of 2-input XOR equation (2mks)

QUESTION FIVE (20 marks)

- a) Explain the associative law of boolean algebra (2mks)
- b) Explain the implementation of 3-8 decoder using AND gate (5mks)
- c) Use the Karnaugh map to solve the following function

$$F1(x, y, z) = \Sigma(3, 4, 5, 6, 7) \quad (4mks)$$

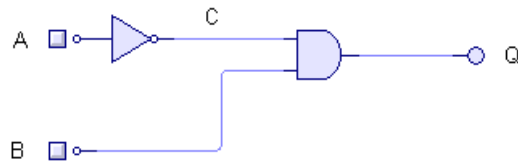- d) Differentiate between leading and trailing edge in clock used for memory elements (2mks)
- e) Draw the half adder circuit and give the equations of the outputs of the sum and carry (3mks)
- f) Study the following logic system carefully and then draw the truth table for it



(4mks)